GENERAL

analog circuits objective questions answers

Published: September 19, 2026 | Index ID: #-

Analog electronics is the backbone of countless modern technologies—ranging from audio amplifiers and radio receivers to medical instrumentation and automotive control systems. Mastering the fundamentals of analog circuits is essential for electrical engineering students, hobbyists, and professionals alike. One of the most effective ways to gauge your understanding and prepare for exams is by tackling a wide range of objective (multiple choice) questions. This article provides a curated set of practice questions, complete answers, and concise explanations covering key topics in analog circuits. Whether you're studying for a certification exam, preparing for an interview, or simply sharpening your skills, this guide will help you build confidence and deepen your conceptual grasp.

Overview of Analog Circuits

Analog circuits process continuous-time signals. Unlike digital circuits that rely on binary states, analog systems manipulate voltage or current that varies smoothly over time. Core components include resistors, capacitors, inductors, transistors, diodes, and operational amplifiers (op amps). Understanding how these elements interact is fundamental to designing amplifiers, filters, oscillators, and signal conditioning circuits.

Basic Electrical Principles

- Ohm's Law: $V = I \times R$
- Kirchhoff's Laws: Current and voltage conservation at nodes and loops
- Capacitance & Inductance: Voltage–current relationships in time domain
- Signal Representation: Time domain vs frequency domain analysis

Common Components

- Resistors: Fixed, variable, and active types (e.g., thermistors, varistors)
- Capacitors: Ceramic, electrolytic, film, and supercapacitors
- Inductors: Air-core, toroidal, and ferrite cores
- Transistors: Bipolar Junction Transistors (BJTs) and Field Effect Transistors (FETs)
- Diodes: Zener, Schottky, and light emitting diodes (LEDs)
- Operational Amplifiers: Inverting, non inverting, differential, and instrumentation amplifiers

Why Practice Objective Questions?

Objective questions offer several advantages for learning analog circuits:

- Immediate Feedback: Correct or incorrect responses help identify knowledge gaps.
- Time Management: Simulate exam conditions to improve speed.
- Conceptual Reinforcement: Repetition of key ideas enhances retention.
- Exam Readiness: Familiarity with question formats reduces test anxiety.

Sample Objective Questions with Answers

Below is a diverse set of 35 objective questions covering foundational and advanced topics. Each question lists four options; the correct answer is indicated in bold. Short explanations follow each answer to clarify reasoning.

Category 1: Basic Electrical Principles

1. Which law states that the total current entering a junction equals the total current leaving it?\\n\\nOhm’s Law
2. Kirchhoff’s Current Law (KCL)
3. Kirchhoff’s Voltage Law (KVL)
4. Faraday’s Law

Explanation: KCL ensures current conservation at a node; the algebraic sum of currents entering a node is zero.

1. 15.9 :•
2. 25.3 :•
3. 159 :•
4. 1590 :•

Impedance Zc = 1 / (2< d2’à Plugging values: 1 / (2< r r s ² b’ $, S’ ©.

1. Resistor
2. Capacitor
3. Inductor
4. Transistor

Transistors are active devices that can amplify or switch signals.

Category 2: Operational Amplifiers

1. In a non inverting op amp configuration, the voltage gain (Av) is given by:\\n\\n1 + (R2 / R1)
2. 1 + (R1 / R2)
3. R2 / R1
4. R1 / R2

The non inverting gain includes the unity gain plus the feedback ratio.

1. Infinite input resistance and zero output resistance
2. Finite input resistance and infinite output resistance
3. Zero input resistance and infinite output resistance
4. Finite input and output resistance

These assumptions simplify analysis and highlight the amplifier’s ideal behavior.

1. To limit the input current
2. To set the closed loop gain
3. To provide power supply decoupling
4. To protect against over voltage

Feedback defines the relationship between input and output, stabilizing the circuit.

Category 3: Filters and Frequency Response

1. Which filter type attenuates frequencies above a specified cutoff frequency?\\n\\nLow pass filter
2. High pass filter
3. Band pass filter
4. Band stop filter

A low pass filter allows low frequencies to pass while attenuating high frequencies.

1. 1 / (2< $2•
2. 1 / (2< !¢…$2’•
3. 1 / (2< $2›

4. 2< $0

The standard RC cutoff formula applies to first order; for second order, the same form holds with effective R and C values.

1. Resistor
2. Capacitor
3. Inductor
4. Diode

Capacitors provide frequency dependent impedance, enabling phase shifts.

Category 4: Oscillators and Signal Generators

1. Which condition must be satisfied for a Wien bridge oscillator to sustain oscillations?\\n\\nAmplitude gain > 1 and phase shift = 0°
2. Amplitude gain = 1 and phase shift = 180°
3. Amplitude gain > 1 and phase shift = 180°
4. Amplitude gain = 1 and phase shift = 0°

The Barkhausen criterion requires unity gain and zero net phase shift.

1. Higher frequency stability
2. Lower cost
3. Higher output power
4. Smaller size

Crystals provide superior frequency precision due to their piezoelectric properties.

1. Frequency of the reference and the VCO
2. Phase of the reference and the VCO
3. Amplitude of the reference and the VCO
4. Current of the reference and the VCO

The phase detector generates an error signal proportional to phase difference.

Category 5: Power Amplifiers

1. Which class of amplifier offers the highest efficiency for audio applications?\\n\\nClass A
2. Class B
3. Class AB
4. Class D

Class D amplifiers use pulse width modulation to achieve efficiencies above 90%.

1. To match impedance between amplifier and speaker
2. To split the audio signal into frequency bands
3. To provide power supply filtering
4. To protect the amplifier from over current

Crossover networks direct low, mid, and high frequencies to appropriate drivers.

1. Gain
2. Impedance
3. Power handling capability
4. Bandwidth

This refers to the amplifier’s ability to output high power safely.

Category 6: Analog to Digital and Digital to Analog Conversion

1. In a successive approximation ADC, the resolution is determined by:\\n\\nThe reference voltage
2. The clock frequency
3. The number of bits in the converter
4. All of the above

Resolution = 2 •, where n is the number of bits.

Baca Juga (Artikel Terkait)

- **advanced engineering electromagnetics solution manual edition hardcover by balanis constantine a published by wiley**
  URL: http://www.ewaroyal.com/advanced-engineering-electromagnetics-solution-manual-edition-hardcover-by-balanis-constantine-a-published-by-wiley.pdf
- **advanced engineering electromagnetics solutions manual**
  URL: http://www.ewaroyal.com/advanced-engineering-electromagnetics-solutions-manual.pdf
- **advanced engineering electromagnetics wiley 1989 grading**
  URL: http://www.ewaroyal.com/advanced-engineering-electromagnetics-wiley-1989-grading.pdf
- **advanced engineering fluid mechanics by biswas**
  URL: http://www.ewaroyal.com/advanced-engineering-fluid-mechanics-by-biswas.pdf

Tags: #analog #circuits #objective